

### Unit-3 (Digital Electronics)

BCD Codes : (Binary Coded Decimal)-Each decimal digit is represented by a 4-bit binary number.

Decimal Number	Binary.	BCD
0	0 0 0 0	0 0 0 0
1	0 0 0 1	0 0 0 1
2	0 0 1 0	0 0 1 0
3	0 0 1 1	0 0 1 1
4	0 1 0 0	0 1 0 0
5	0 1 0 1	0 1 0 1
6	0 1 1 0	0 1 1 0
7	0 1 1 1	0 1 1 1
8	1 0 0 0	1 0 0 0
9	1 0 0 1	1 0 0 1
10	1 0 1 0	0 0 0 1 0 0 0 0
11	1 0 1 1	0 0 0 1 0 0 0 1
12	1 1 0 0	0 0 0 1 0 0 1 0
13	1 1 0 1	0 0 0 1 0 0 1 1
14	1 1 1 0	0 0 0 1 0 1 0 0
15	1 1 1 1	0 0 0 1 0 1 0 1

Convert the following decimal numbers to BCD

(a) - 35

(b) 174

(c) 2479

Gray to

Excess-3 Code: It's a modified

form of a BCD number. It can be derived from the natural BCD by adding 3 to each Coded number.

	<del>Excess-3</del> 0011
0	0100
1	0101
2	0110
3	0111
4	1000
5	1001
6	1010
7	1011
8	1101

Ex

Gray Code: It is a special unit-distance code. In this code bit patterns for two consecutive numbers differ in only one bit position. These codes are also called cyclic codes.

Binary to Gray Code Conversion

Binary  $\rightarrow B_1 \oplus B_2 \oplus B_3 \oplus B_4$


Ex       $\begin{matrix} & \downarrow & \downarrow & \downarrow & \downarrow \\ G_1 & G_2 & G_3 & G_4 \end{matrix}$

$$\begin{matrix} 1 & \oplus & 0 & \oplus & 1 & \oplus & 1 & \oplus & 1 & \oplus & 0 & \oplus & 1 & \oplus & 1 \\ \downarrow & & \downarrow \\ 1 & & 1 & & 1 & & 0 & & 0 & & 1 & & 1 & & 0 \end{matrix}$$


Basic  
① AND  
② OR  
③ NOT  
④ XOR  
⑤ XNOR  
⑥ AND-NOT  
⑦ OR-NOT  
⑧ NOT-AND  
⑨ NOT-OR

fixed  
derived  
to each

## Gray to Binary

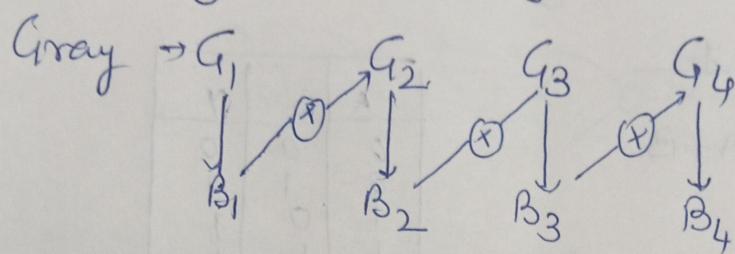

Ex

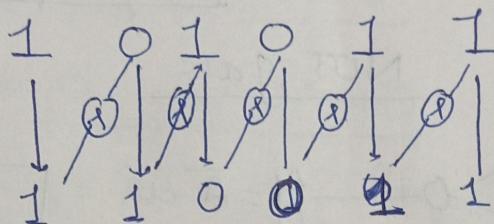

## Logic gates

### Basic gates


- ① AND
- ② OR
- ③ ~~NOT~~
- ④ ~~EX-NOR~~
- ⑤ EX-OR
- ⑥ EX-NOR
- ⑦ NOT.

### Universal gates

- ① NAND
- ② NOR

By using Universal  
gates any basic gates.  
Can be formed.


### AND gate

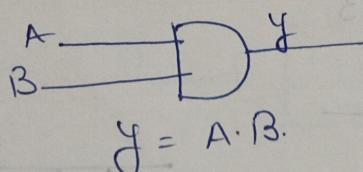

### Truth Table


A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

### OR gate

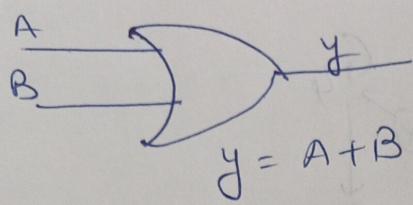


A	B	y
0	0	0
0	1	1
1	0	1
1	1	1

### NOT gate

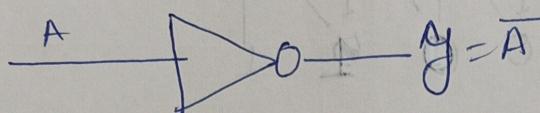


A	y
0	1
1	0

### Ex-OR

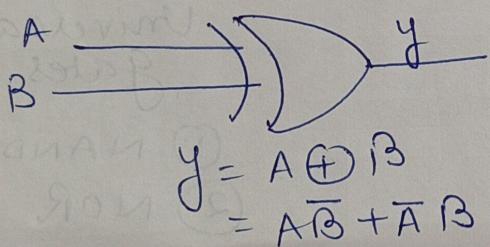


A	B	y
0	0	0
0	1	1
1	0	1
1	1	0

### Ex-NOR

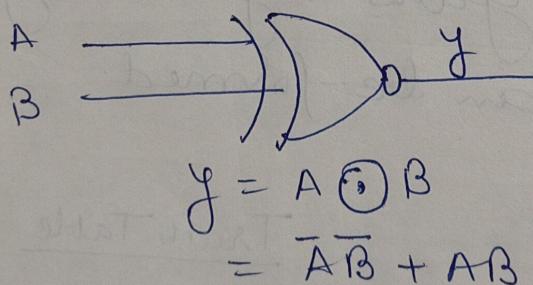


A	B	y
0	0	1
0	1	0
1	0	0
1	1	1

### NAND

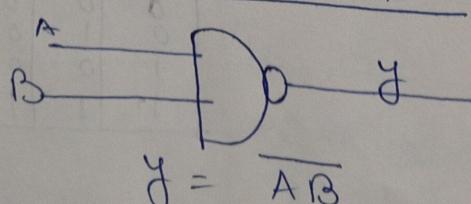

A	B	y
0	0	1
0	1	1
1	0	1
1	1	0

## NOR

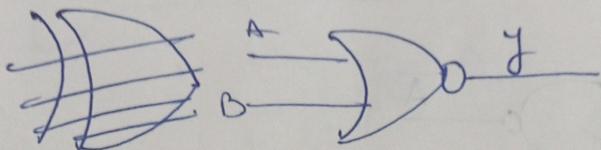


A	B	y
0	0	1
0	1	0
1	0	0
1	1	0

## Conversion of Gates

### 1) - NAND to AND

Given  $y = \overline{AB}$

Required  $y = AB$

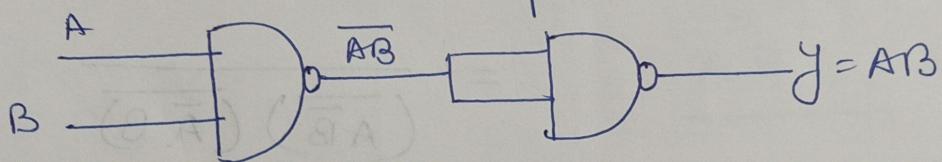


### 2) - NAND to OR

$$y = \overline{AB}$$


$$\begin{aligned} \bar{y} &= \overline{\overline{AB}} \\ &= \overline{A} + \overline{B} \\ &= \overline{A} + \overline{B} \end{aligned}$$

$$y = A + B$$
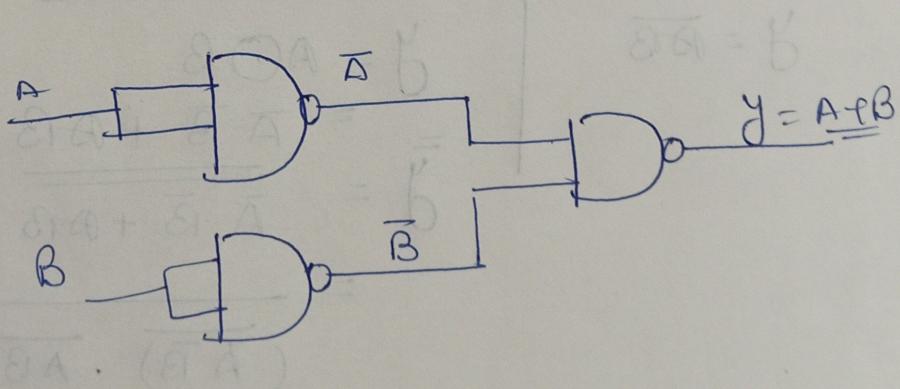
$$\begin{aligned} \bar{y} &= \overline{A + B} \\ &= \overline{\overline{A} + \overline{B}} \\ &= \overline{\overline{A}} + \overline{\overline{B}} \\ &= \overline{A} + \overline{B} \end{aligned}$$



### NAND to NOT

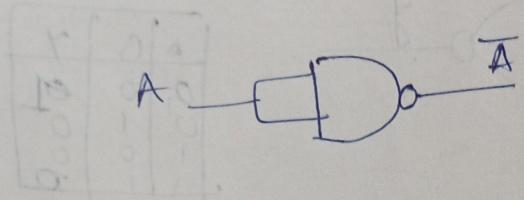

### NAND to Ex-OR


$$y = \overline{AB}$$

$$y = A \oplus B$$

$$= A\bar{B} + \bar{A}B$$

$$\bar{y} = \overline{\overline{AB} + \bar{A}B}$$
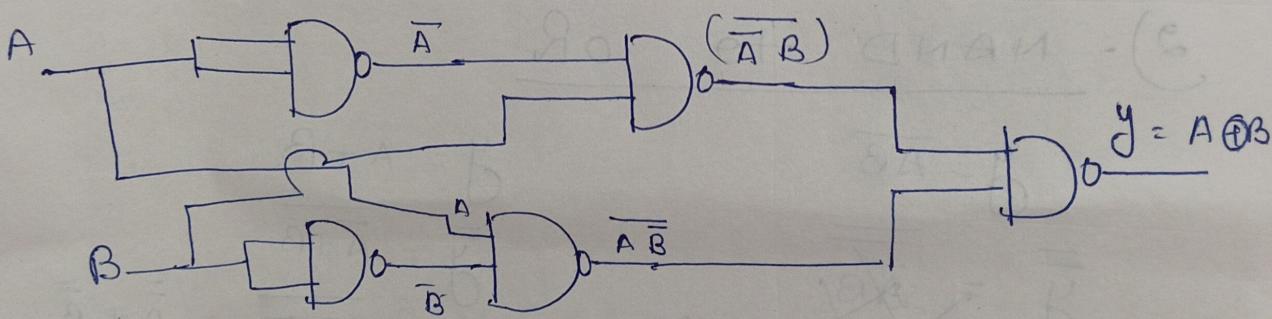
$$= \overline{(\overline{AB}) (\bar{A}B)}$$



### NAND to Ex-NOR


$$y = \overline{AB}$$

$$y = A \odot B$$

$$= \overline{A\bar{B} + \bar{A}B}$$

$$\bar{y} = \overline{\overline{A\bar{B}} + \overline{\bar{A}B}}$$
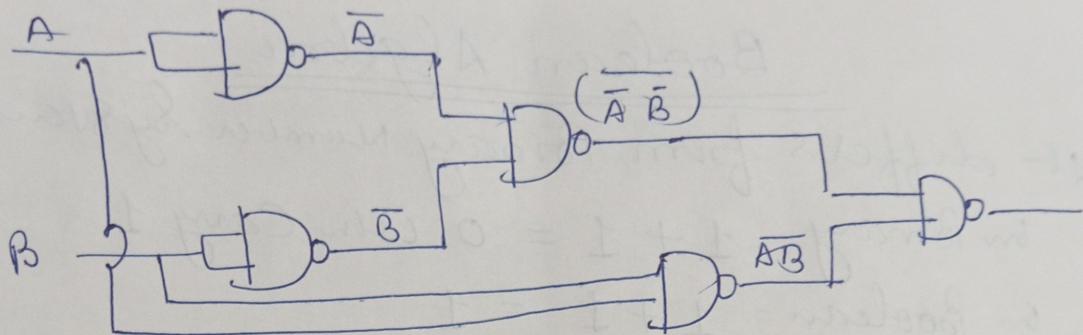
$$= \overline{(\overline{A\bar{B}}) \cdot (\overline{\bar{A}B})}$$



NAND TO NOR

$$Y = \overline{AB}$$

$$Y = \overline{A + B}$$

$$(S \cdot B) \cdot A = S \cdot (A \cdot A)$$


$$(S \cdot B) + A = S + (B + A)$$

$$SA + BA = (S + B)A$$

$$\overline{Y} = \overline{\overline{A} + \overline{B}}$$

$$\overline{Y} = \overline{\overline{A} + \overline{B}} = \overline{\overline{A} \overline{B}}$$
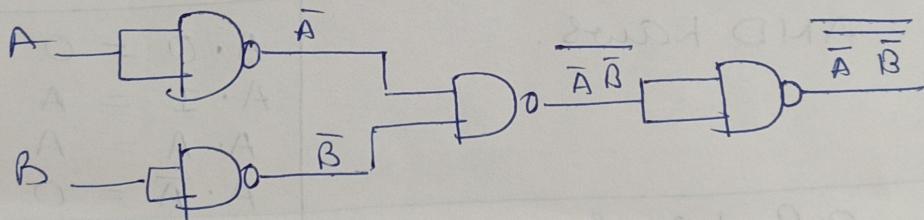
$$= \overline{\overline{A} \overline{B}}$$



Similarly, NOR TO AND, OR, NOT, EX-OR, EX-NOR, NAND

$$A = A + A$$

$$A = \overline{A} + A$$

$$A = \overline{A}$$

$$(S \cdot A)(S + A) = SA + A$$

$$B + \overline{A} = B \cdot A + \overline{A}$$

$$B + \overline{A} = \overline{B} \cdot A + \overline{A}$$

$$A = \overline{B} \cdot A + A$$

$$B + A = \overline{B} \cdot A + A$$

## Boolean Algebra

It differs from Binary Number System

In Binary:  $1 + 1 = 0$  with carry 1

In Boolean:  $1 + 1 = 1$

### Boolean Algebra Laws

S. No.	Name of Law	Statement
1 -	Commutative Law	$A \cdot B = B \cdot A$ $A + B = B + A$
2.	Associative law.	$(A \cdot B) \cdot C = A \cdot (B \cdot C)$ $(A + B) + C = A + (B + C)$
3.	Distributive law.	$A(B+C) = AB+AC$
4	AND laws.	$A \cdot 0 = 0$ $A \cdot 1 = A$ $A \cdot A = A$ $A \cdot \bar{A} = 0$
5	OR Laws	$A + 0 = A$ $A + 1 = 1$ $A + A = A$ $A + \bar{A} = 1$
6	Inversion laws	$\bar{\bar{A}} = A$
7	Other Important laws.	$A + BC = (A+B)(A+C)$ $\bar{A} + A\bar{B} = \bar{A} + B$ $\bar{A} + A\bar{B} = \bar{A} + \bar{B}$ $A + AB = A$ $A + \bar{A}B = A + B$

## De Morgan's theorems

$$\textcircled{1} \quad \overline{A \cdot B} = \overline{A} + \overline{B}$$

$$\textcircled{2} \quad \overline{A + B} = \overline{A} \cdot \overline{B}$$

$$\underline{\text{Ex}} \quad A + BC = (A+B)(A+C)$$

$$\underline{\text{L.H.S.}} \quad A + BC$$

$$\Rightarrow A \cdot 1 + BC$$

$$\Rightarrow A \cdot (1+C) + BC$$

$$\Rightarrow A \cdot 1 + AC + BC$$

$$\Rightarrow \cancel{A \cdot 1} + C(A+B)$$

$$= A \cdot (1+B) + AC + BC$$

$$= A \cdot 1 + AB + AC + BC$$

$$= A \cdot A + \underline{AB} + AC + BC$$

$$= A \cdot A + AC + \cancel{AB} + BC$$

$$= A(A+C) + B(A+C)$$

$$= \underline{(A+C)(A+B)}$$

$$\underline{\text{Q.}} \rightarrow \textcircled{1} \quad A + AB = A$$

$$\textcircled{2} \quad A + \overline{A}B = A + B$$

$$\textcircled{3} \quad (A+B)(A+C) = A+BC$$

$$\textcircled{4} \quad (\cancel{A+\overline{B}}) / ((A+\overline{B}) + AB) (A+\overline{B}) (\overline{A}B) = 0$$

$$\textcircled{5} \quad A + \overline{A}B + AB = A + B$$

$$\textcircled{6} \quad ABCD + A\overline{B}CD = ACD$$

$$\textcircled{7} \quad (\overline{AB} + \overline{A} + AB) = 0$$

$$\textcircled{8} \quad AB + ABC + A\overline{B} = A$$

## SOP & POS Representation

for logic Expression

SOP Form. (Sum of Product)

$$Y = A \cdot B + A \cdot C + B \cdot C$$

product terms

$$Y = \overline{A} \cdot B \cdot \overline{C} + A \cdot \overline{B} \cdot \overline{C} + \overline{A} \cdot \overline{B} \cdot \overline{C}$$

POS Form (Product of Sum)

$$Y = (A + B) \cdot (B + \overline{C}) \cdot (\overline{A} + B)$$

Standard or Canonical SOP & POS forms

$$\text{Standard SOP} \rightarrow Y = f(A, B, C)$$

$$= \underbrace{A \cdot B \cdot C}_{\text{minterm 1}} + \underbrace{A \cdot \overline{B} \cdot C}_{\text{minterm 2}} + \underbrace{\overline{A} \cdot B \cdot C}_{\text{minterm 3}}$$

All terms have all variables either in its original form or in its complemented form.

$$Y = AB + \overline{B}C + \overline{A}$$

Convert into Standard form.

$$Y = AB(C + \overline{C}) + (A + \overline{A}) \cdot \overline{B}C + \overline{A}(B + \overline{B}) \cdot C$$

$$= ABC + AB\overline{C} + A\overline{B}C + \overline{A}\overline{B}C + \overline{ABC} + \overline{A}BC + \overline{AB}\overline{C} + \overline{A}\overline{B}\overline{C}$$

## Standard POS form

$$Y = \frac{(A + B + \bar{C})}{\text{max term 1}} \cdot \frac{(A + \bar{B} + C)}{\text{max term 2}} \cdot \frac{(\bar{A} + \bar{B} + \bar{C})}{\text{max term 2}}$$

$$Y = (A + B) (A + C) C \bar{A}$$

$$= (A + B + 0) (A + C + 0) (\bar{A} + 0)$$

$$= (A + B + C \bar{C}) (A + C + B \bar{B}) (\bar{A} + B \bar{B} + \cancel{C \bar{C}})$$

$$= (A + B + C) (A + B + \bar{C}) (A + C + B) (A + C + \bar{B})$$

$$(A + B + C) (A + \bar{B} + C)$$

Minterms & Max terms for 3 variables

Variables			Minterms	Maxterms
0	0	0	$\bar{A} \bar{B} \bar{C} = m_0$	$A + B + C = M_0$
0	0	1	$\bar{A} \bar{B} C = m_1$	$A + B + \bar{C} = M_1$
0	1	0	$\bar{A} B \bar{C} = m_2$	$A + \bar{B} + C = M_2$
0	1	1	$\bar{A} B C = m_3$	$A + \bar{B} + \bar{C} = M_3$
1	0	0	$A \bar{B} \bar{C} = m_4$	$\bar{A} + B + C = M_4$
1	0	1	$A \bar{B} C = m_5$	$\bar{A} + B + \bar{C} = M_5$
1	1	0	$A B \bar{C} = m_6$	$\bar{A} + \bar{B} + C = M_6$
1	1	1	$A B C = m_7$	$\bar{A} + \bar{B} + \bar{C} = M_7$

$$y = \underline{A\bar{B}C} + \bar{A}\bar{B}c + A\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C}$$

$$= m_5 + m_1 + m_4 + m_0$$

$$= m_0 + m_1 + m_4 + m_5$$

$$\boxed{y = \sum m(0, 1, 4, 5)}$$

$$y = (A + \bar{B} + c) (\bar{A} + \bar{B} + c) (A + \bar{B} + \bar{C})$$

$$(\bar{A} + \bar{B} + \bar{C})$$

$$= M_2 \cdot M_6 \cdot M_3 \cdot M_7$$

$$\boxed{y = \prod M(2, 3, 6, 7)}$$

### K-MAP

K-map is used to minimize the boolean function.

K-map for 3 variables.

		BC				
		00	01	11	10	
		0	0	1	3	2
		1	4	5	7	6

K-map for 4 variables

		CD				
		00	01	11	10	
		00	0	1	3	2
		01	4	5	7	6
		11	12	13	15	14
		10	8	9	11	10

$$\text{Ex} \quad y = \sum m(0, 1, 2, 5, 13, 15)$$

$$\text{Ans. } \overline{A}\overline{B}\overline{D} + \overline{A}\overline{C}D + ABD$$

$$y = \sum m(1, 5, 7, 9, 11, 13, 15)$$

$$\text{Ans. } \overline{A}D + BD + AD$$

$$y = \sum m(1, 3, 5, 9, 11, 13)$$

$$y = \overline{B}D + \overline{C}D$$

\$

$$y = \sum m(1, 2, 3, 4, 5, 7, 9, 11, 13, 15)$$

$$y = \overline{A}\overline{B}\overline{C} + D$$

$$y = \sum m(1, 2, 9, 10, 11, 14, 15)$$

$$\text{Ans. } \overline{B}(C \oplus D) + AC$$

$$y = \sum m(4, 5, 8, 9, 11, 12, 13, 15)$$

$$\text{Ans. } \overline{C}(A+B) + AD$$

$$y = \sum m(1, 3, 7, 11, 15) + d(0, 2, 5)$$

$$y = CD + \overline{A}\overline{B}$$


$$y = \sum m(0, 1, 5, 9, 13, 14, 15) + d(3, 4, 7, 10, 11)$$

$$\text{Ans. } (D + (A \odot C))$$

$$y = \prod M(0, 2, 3, 5, 7)$$


$$\text{Ans. } (A+C)(\overline{A}+\overline{C})(\overline{B}+\overline{C})$$

## Combinational Circuits

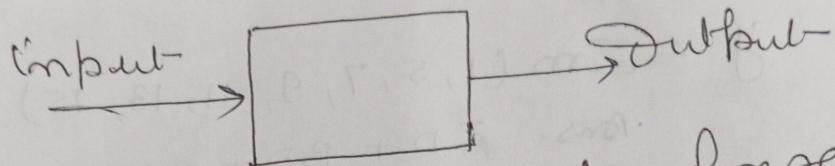

Output is only depend upon present input  
there is no memory element.


### Half Adder

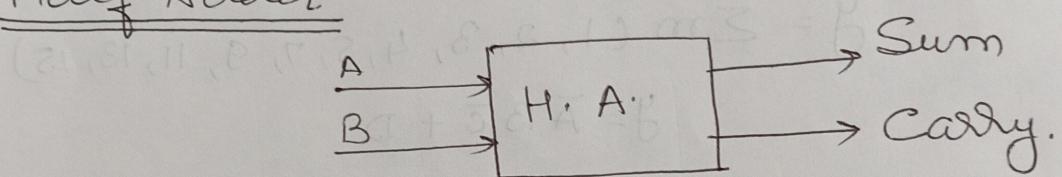


A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$\begin{aligned} \text{Sum} &= \overline{A}B + A\overline{B} \\ &= A \oplus B \end{aligned}$$

$$\text{Carry} = AB$$

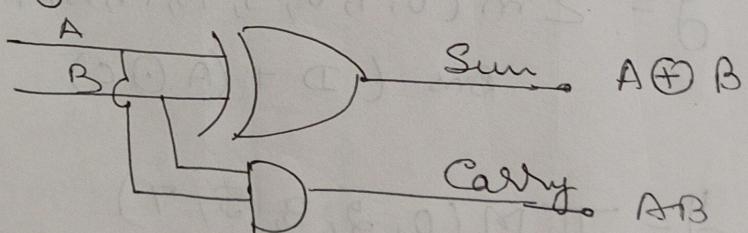


## Full Adder

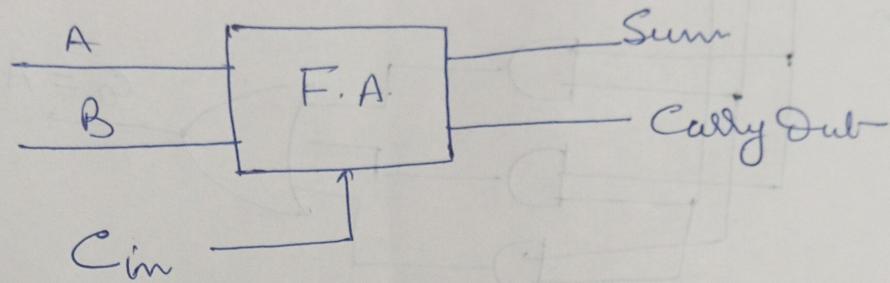


A	B	Cin	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$\begin{aligned}
 S &= \overline{A} \overline{B} C_{in} + \overline{A} B \overline{C}_{in} + A \overline{B} \overline{C}_{in} + AB C_{in} \\
 &= (\overline{A} \overline{B} + AB) C_{in} + (\overline{A} B + A \overline{B}) \overline{C}_{in} \\
 &= (\overline{A} B + A \overline{B}) C_{in} + (\overline{A} B + A \overline{B}) \overline{C}_{in} \\
 &= \overline{A} \oplus B \oplus C_{in}
 \end{aligned}$$

$$\begin{aligned}
 C &= \overline{A} B C_{in} + A \overline{B} C_{in} + A B \overline{C}_{in} + AB C_{in} \\
 &= \overline{A} B C_{in} + \underline{A \overline{B} C_{in}} + \underline{A B C_{in}} + A B \overline{C}_{in} \\
 &= \overline{A} B C_{in} + A C_{in} + A B \overline{C}_{in} \\
 &= (A + B) C_{in} + A B \overline{C}_{in} \\
 &= A C_{in} + B C_{in} + A B \overline{C}_{in} \\
 &= \overline{A} \overline{B} (B + C_{in}) + B C_{in} \\
 &\quad \overline{A} B + A C_{in} + B C_{in}
 \end{aligned}$$

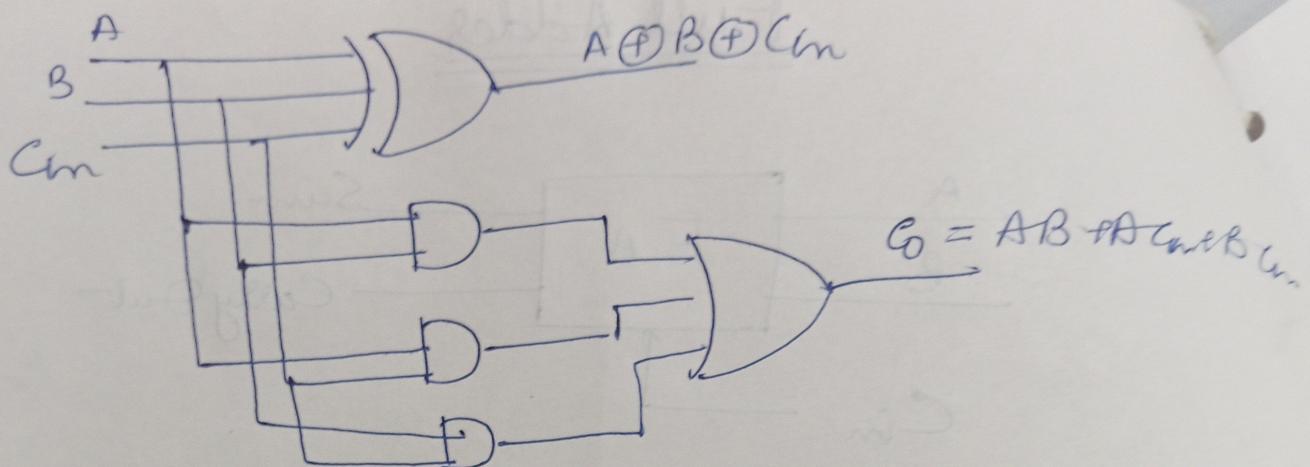

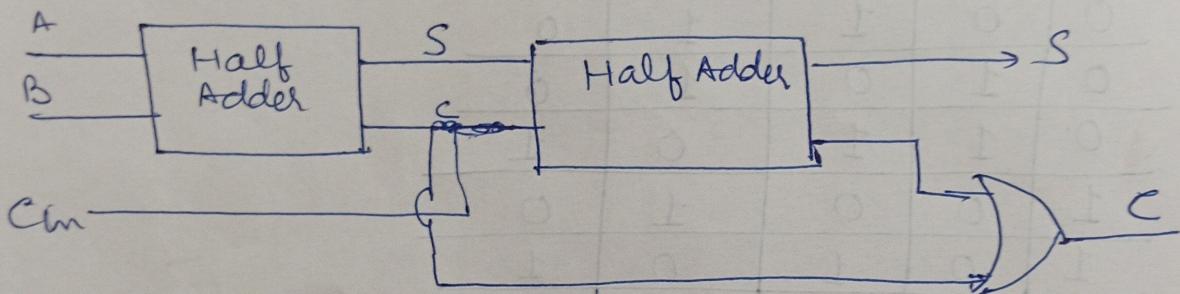Construction of full adder using Half Adder



### Binary Subtractor


$$0 - 0 = 0, \quad 0 - 1 = 1 \text{ with borrow}_1$$

$$1 - 0 = 1, \quad 1 - 1 = 0$$

Half Subtractor:

$$D = \overline{A}B + A\overline{B}$$

$$B = A\overline{B}$$

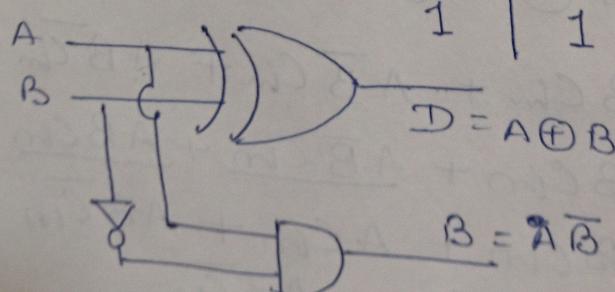

A	B	D	B
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	0

## Full Subtractor

A	B	$B_m$	D	$B_o$
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

$A \quad B \quad B_m$

	00	01	11	10
0	(1)			(1)
1	(1)		(1)	

$A \quad B \quad B_m$

	00	01	11	10
0		(1)	(1)	(1)
1			(1)	

$$\begin{aligned}
 D &= A \bar{B} \bar{B}_m + \bar{A} \bar{B} B_m + AB \bar{B}_m + \bar{A} B \bar{B}_m \\
 &= A \oplus B \oplus B_m.
 \end{aligned}$$

$$B_{out} = \bar{A} B_m + \bar{A} B + B \bar{B}_m.$$

